


## → Combinational circuits :-

In this type of circuit, output of the circuit only depended ~~only~~ upon input values.

It does not use any memory.

It is type of logic circuit.

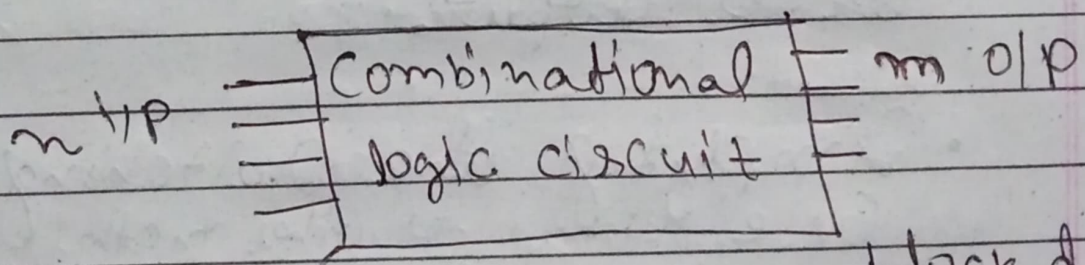It has  $n$ -input and will have  $m$  ~~corresponding~~ output.



block diagram

ex. - adder, subtractor, converter, encoder/decoder etc.


## Steps to construct combinational logic circuit from boolean expression.

- From expression or problem, identify inputs and outputs and draw a block diagram.
- Draw a truth table such that the problem completely describes the operation of the circuit for different combinations.
- Write down the switching expression ~~or~~ for outputs.
- Simplify the switching expression (use k-map or other method).
- Implement the simplified expression using logic gates.


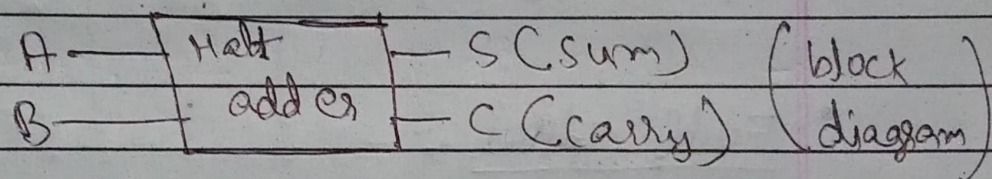
## • Half-adder :-

It is a simple combination of circuits to perform arithmetic addition of two binary digits.



T. T.

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

(Truth table)

we will only consider those condition  
'In which result is '1'

So,


$$S = \overline{A}B + A\overline{B}$$

$$= A \oplus B$$

$$C = AB$$

(Switching  
expression  
for output)




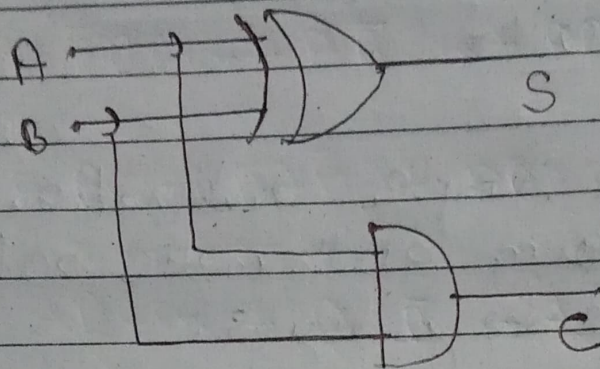
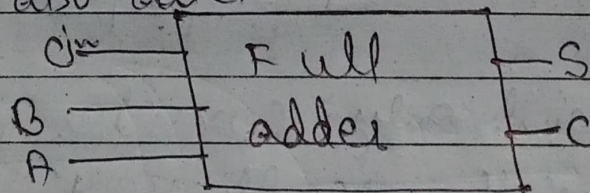
### • Full adder:-

It is a combinational logic circuit in which 3 bit numbers are added and we get sum and carry as output.

In this problem lower order carry ~~is~~ also added.



A, B  $\rightarrow$  ~~Two input to add~~ Two Significant bit.  
 $\left[ \begin{array}{c} \text{Carry of} \\ \text{cin} \end{array} \right] \rightarrow$  previous lower Significant ~~carry~~ bit (A+B)



input			Output	
A	B	Cin	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Switching expression of output is made by summing all input for which output is 1.

$$S = \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + AB\bar{C}_{in}$$

$$= \bar{A}(\bar{B}C_{in} + B\bar{C}_{in}) + A(\bar{B}\bar{C}_{in} + BC_{in})$$

$$= \bar{A}(B \oplus C_{in}) + A(\overline{B \oplus C_{in}})$$

$$\text{Let } B \oplus C_{in} = X \quad \text{--- (1)}$$

~~Can~~

$$= \bar{A}X + A\bar{X}$$

$$= A \oplus X$$

$$= \underline{A \oplus B \oplus C_{in}} \quad (\text{from (1)})$$

$$C = \bar{A}BC_{in} + A\bar{B}C_{in} + AB\bar{C}_{in} + ABC_{in}$$

$$= BC_{in}(A + \bar{A}) + A\bar{B}C_{in} + AB\bar{C}_{in}$$

$$= BC_{in} + A(\bar{B}C_{in} + B\bar{C}_{in})$$

$$= BC_{in} + A(B \oplus C_{in})$$


$$= BC_{in} + A\bar{B}C_{in} + AB\bar{C}_{in}$$

$ABC_{in}$  term is twice added to simplify-

$$C = BC_{in} + A\bar{B}C_{in} + \cancel{ABC_{in}} + AB\bar{C}_{in} + \cancel{ABC_{in}}$$


$$= BC_{in} + AC_{in}(B + \bar{B}) + AB(\bar{C}_{in} + C_{in})$$

$$= BC_{in} + AC_{in} + AB$$

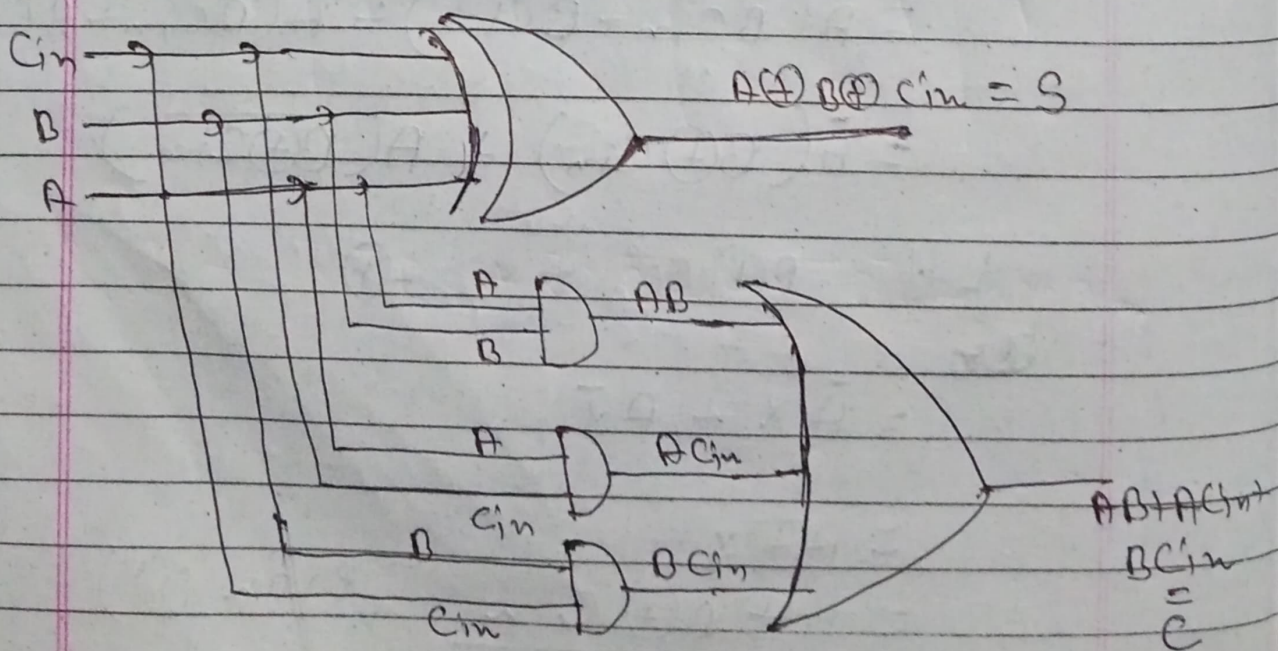



• Half Subtractor :-

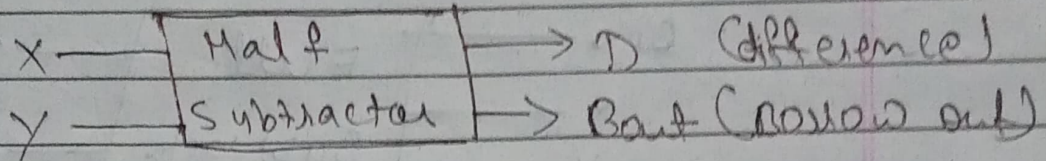

T.T.

X	Y	D	Bout
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

So,

$$D = \bar{X}Y + X\bar{Y}$$

$$= X \oplus Y$$

$$Bout = \bar{X}Y$$

